

补充作业1:

□ 四名学生 (A, B, C, D) 申请出国奖学金, 现有如下条件需要满足:

■ ① A和B至少有一人被选中;

$$\bar{A}B + A\bar{B} + AB$$

$$A + B$$

■ ② A和D不能同时被选中;

$$\bar{A}D + A\bar{D} + \bar{A}\bar{D}$$

$$\bar{AD}$$

■ ③ C和D中有且只有一人获得奖学金;

$$\bar{C}D + C\bar{D}$$

■ ④ B和C或者同时获得奖学金, 或者同时失去奖学金;

$$BC + \bar{B}\bar{C}$$

□ 请写出申请结果的逻辑表达式并化简为最简与或式。

补充作业1:

思路1: $F = (\bar{A}B + A\bar{B} + AB)(\bar{A}D + A\bar{D} + \bar{A}\bar{D})(\bar{C}D + C\bar{D})(BC + \bar{B}\bar{C})$

思路2: $F = (A + B)(\bar{A} + \bar{D})(\bar{C}D + C\bar{D})(BC + \bar{B}\bar{C})$

$$\bar{F} = \bar{A}\bar{B} + AD + CD + \bar{C}\bar{D} + \bar{B}\bar{C} + \bar{B}C$$

F 的卡诺图

	CD			
AB	00	01	11	10
00	0	0	0	0
01	0	0	0	1
11	0	0	0	1
10	0	0	0	0

补充作业1:

思路1: $F = (\bar{A}B + A\bar{B} + AB)(\bar{A}D + A\bar{D} + \bar{A}\bar{D})(\bar{C}D + C\bar{D})(BC + \bar{B}\bar{C})$

思路2: $F = (A + B)(\bar{A} + \bar{D})(\bar{C}D + C\bar{D})(BC + \bar{B}\bar{C})$

$$\bar{F} = \bar{A}\bar{B} + AD + CD + \bar{C}\bar{D} + B\bar{C} + \bar{B}C$$

F的卡诺图

$$F = BC\bar{D}$$


CD \ AB		00	01	11	10
AB	00	0	0	0	0
	01	0	0	0	1
	11	0	0	0	1
	10	0	0	0	0

补充作业2:

仅用一片74LS138设计地址译码器，译出输入地址 $A_7, \dots, A_0 = 98H, \dots, 9FH$ 。

思路:




8根输入地址线的可能取值范围是00H...FFH

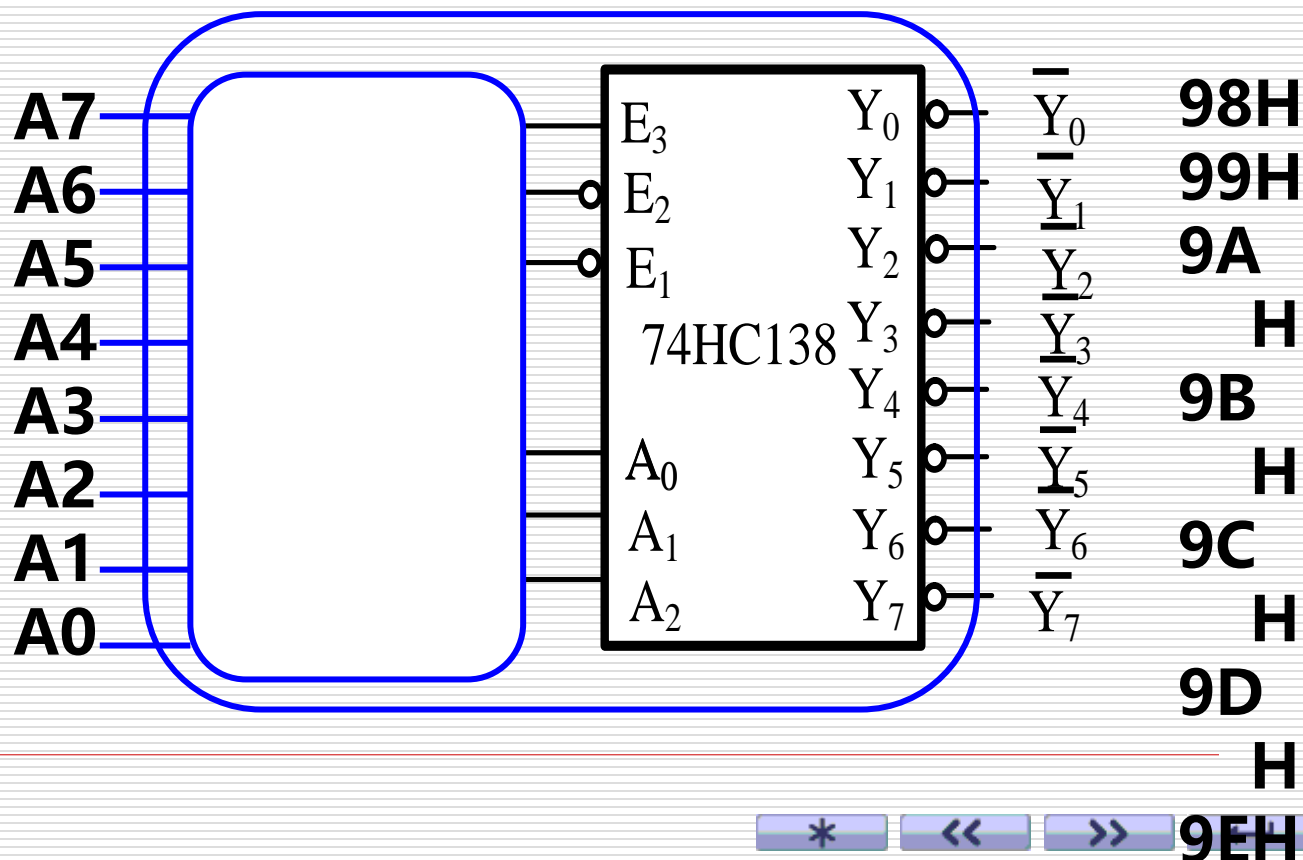

补充作业2:

思路： 98H,...,9FH理解为8个地址（房间号）。片内译码就是要利用8个输入信号中发生变化的bit，观察可发现：
A7,...,A3 没有发生变化，所以利用A2,...,A0 连接138的CBA实现地址译码，利用高五位产生片选信号，当且仅当[A7,...,A3]=10011时本片138使能

片地址=?

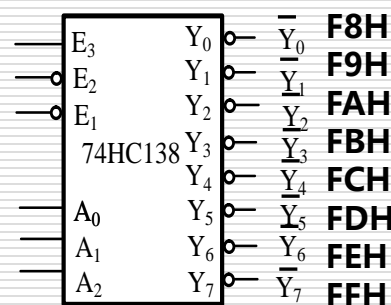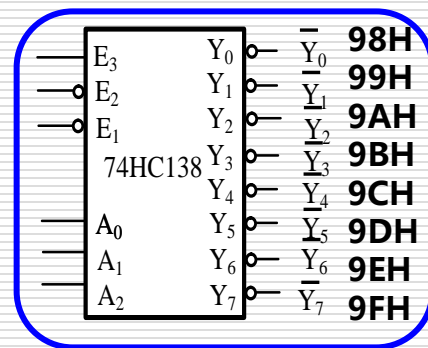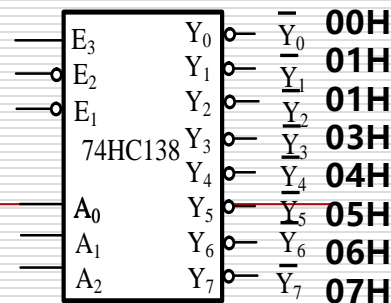

补充作业3：


**仅用全加器组成八位二进制代码奇校验器，
电路应如何连接？**

补充作业3:

全加器组成的八位二进制代码奇偶校验器

$$L = b_7 \oplus b_6 \oplus b_5 \oplus b_4 \oplus b_3 \oplus b_2 \oplus b_1 \oplus b_0$$

S_{i-3}	S_{i-2}	S_{i-1}	L
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

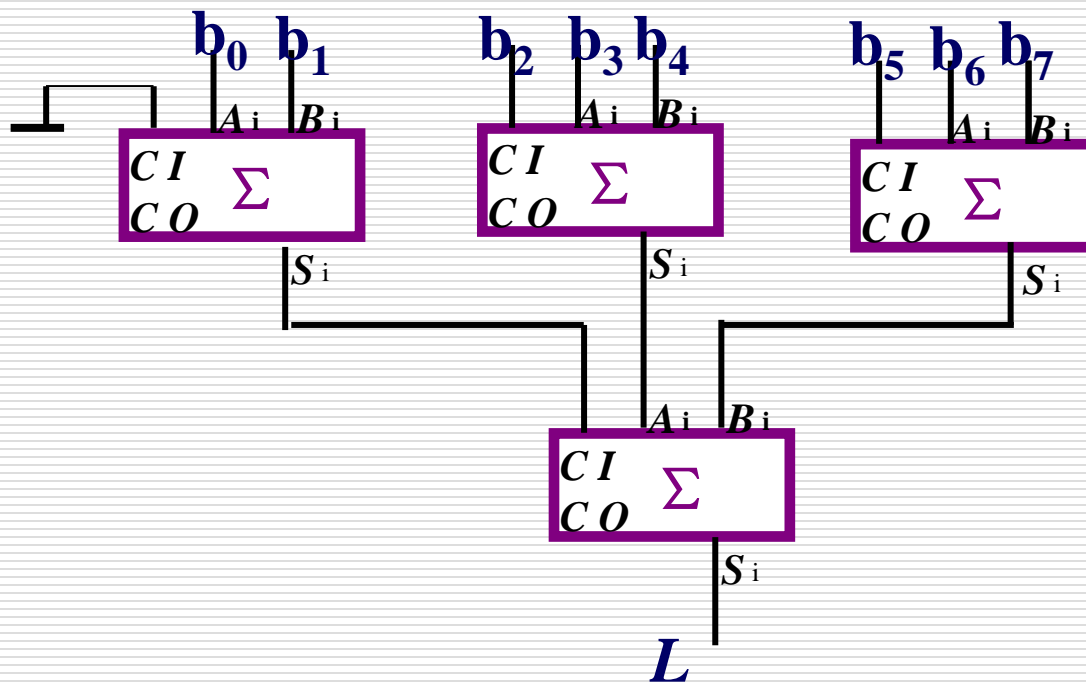

补充作业4:

试仅用一片74LS151，不加任何门电路实现逻辑函数：

$$F(ABCD) = \sum m(2,5,6,7,8,10,11,12,14,15)$$

思路与前一题类似

$$F = C\bar{D} + A\bar{D} + AC + \bar{A}BD + BC$$

选择A、C、D作为通道选择信号，**A为最高位**

$$\begin{aligned} F &= C\bar{D} + A\bar{D} + AC + \bar{A}BD + BC \\ &= \bar{A}C\bar{D} + A\bar{C}\bar{D} + ACD + AC\bar{D} + \bar{A}CDB + A\bar{C}DB \end{aligned}$$

D0---D7:0 B 1 B 1 0 1 1

补充作业5:

目前闰年的判定准则可简要归纳为“非百能被4整除，整百能被400整除”。一种verilogHDL实现参考代码如下。其中year_bcd[15:0]存放已通过合法性检查的4位年份对应的BCD码。当输入为闰年时，输出低电平有效的闰年指示leap_year_n。跟据给出的判决思路，填写代码中划线部分；

```
module bcd_div_by_4(bcd,div_by_4);  
    input [4:0]bcd;                // two bcd codes: [7:4]= tens digit,[3:0]=units digit  
    output div_by_4;                // can be divided by 4 when 1  
    _____;                    
  
    always @(*)  
    begin  
        if(bcd[4])                  // odd  
            div_by_4 = (bcd[3:0] == _____)|(bcd[3:0] == _____);  
        else                        // even  
            div_by_4 = (bcd[3:0] == 4'd0)|(bcd[3:0] == 4'd4)|(bcd[3:0] == 4'd8);  
    end  
endmodule  
  
module leap_year_judge(year_bcd,leap_year_n);  
    input [15:0]year_bcd;           //four bcd codes: [15:12]=thousands digit,[11:8]=hundreds  
    digit,[7:4]= tens digit,[3:0]=units digit  
    output leap_year_n;             // 0: leap_year, 1:common year  
    _____  
  
    wire div_by_100,div_by_4,div_by_4_wh; //whole hundreds can be divided by 4  
    bcd_div_by_4 year_bcd_div_by_4(.bcd(year_bcd[4:0]),.div_by_4(div_by_4));  
    bcd_div_by_4 whole_hundred_div_by_4(.bcd(year_bcd[12:8]),.div_by_4(div_by_4_wh));  
    assign div_by_100 = (year_bcd[7:4] == 4'h0) & (year_bcd[3:0] == 4'h0);  
    assign leap_year_n = ~((_____)|(_____));  
endmodule
```

```

module bcd_div_by_4(bcd,div_by_4);
    input [4:0]bcd;           // two bcd codes: [7:4]= tens digit,[3:0]=units digit
    output div_by_4;         // can be divided by 4 when 1
    reg div_by_4;

    always @(*)
    begin
        if(bcd[4])           // odd
            div_by_4 = (bcd[3:0] == 4'd2)|(bcd[3:0] == 4'd6);
        else                 // even
            div_by_4 = (bcd[3:0] == 4'd0)|(bcd[3:0] == 4'd4)|(bcd[3:0] == 4'd8);
        end
    endmodule

    <

module leap_year_judge(year_bcd,leap_year_n);
    input [15:0]year_bcd;     //four bcd codes: [15:12]=thousands digit,[11:8]=hundreds
    digit,[7:4]= tens digit,[3:0]=units digit
    output leap_year_n;       // 0: leap_year, 1:common year
    <

    wire div_by_100,div_by_4,div_by_4_wh; //whole hundreds can be divided by 4
    bcd_div_by_4_year_bcd_div_by_4(.bcd(year_bcd[4:0]),div_by_4(div_by_4));
    bcd_div_by_4_whole_hundred_div_by_4(.bcd(year_bcd[12:8]),div_by_4(div_by_4_wh));
    assign div_by_100 = (year_bcd[7:4] == 4'h0) & (year_bcd[3:0] == 4'h0);
    assign leap_year_n = ~(((~div_by_100) & div_by_4)|(div_by_100 & div_by_4_wh));
    endmodule
    <

```

